

Indian Institute of Technology Delhi
ELL201/ELP201: Digital Electronics Laboratory
2021-22, Semester II
Assignment 2: Verilog Simulations - Counters

Counters are used in a variety of applications in the digital domain. In this experiment, you will be learning the design of two types of counters.

1. Synchronous 4-bit Gray-Code Counter:

A Gray-Code counter counts in such a manner that the difference between any two consecutive states only differs by 1 bit. It is used in a variety of scenarios especially where bit variations/state changes are prohibitive in terms of resource costs.

You can count in any manner, but it should cover all 16 states of the counter in a cyclic manner.

- First, make a state table for the scheme that your counter follows.
- Calculate the number of SR Flip-Flops required.
- Assign values to the inputs S, R for each of the Flip-Flops.
- Use Karnaugh Maps to achieve minimized expressions for the inputs.
- Write Verilog code for this counter.

Hint: Make an entity for SR Flip-Flop, use these as components in your counter, and assign inputs to these Flip-Flops depending on the minimized expressions achieved as a function of the current outputs. Ensure your Flip-Flop is either positive- or negative- edge triggered and does not function as a Latch).

2. Synchronous Ring Counter:

A Ring counter behaves like a Shift-Register, except that the first Flip-Flop gets an input which can be a combination of any of the current states. Johnson Counter that is covered in class, is an example of a Ring Counter.

- First, calculate the number of D Flip-Flops required.
- Assign values to the inputs D for each of the Flip-Flops looking at the state table (Fig. 1). Note that for the intermediate flip-flops, the behaviour is the output of one fed as input to the other. Be careful about the input of the MSB of the states.

- When implementing the counter, let it start from the state **b4b3b2b1** where **b4b3b2b1** is 4-bit binary representation of **X4**, and **X4** is last digit of your Entry no. 2020EE1X1X2X3X4.
- Write Verilog code for this counter.
(Hint: Make an entity for D Flip-Flop, use these as components in your counter, and assign inputs to these Flip-Flops depending on the behaviour deduced from the state table. Ensure your Flip-Flop is either positive- or negative-edge triggered, and does not function as a Latch)
- Does the counter cover all 16 possible states? Try to figure out what the counter is trying to do, and how it depends on which state the counter starts from.

Q3	Q2	Q1	Q0	D3	D2	D1	D0
0	0	0	1	1	0	0	0
1	0	0	0	0	1	0	0
0	1	0	0	0	0	1	0
0	0	1	0	1	0	0	1
1	0	0	1	1	1	0	0
1	1	0	0	0	1	1	0
0	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1
0	1	0	1	1	0	1	0
1	0	1	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1
0	0	1	1	0	0	0	1

Figure 1: State Table for Synchronous Ring Counter