

ELP201 Lab Report 2

Adit Malhotra

2020EE10458

1 Synchronous 4-bit Gray-Code Counter

1.1 Counter Scheme

The scheme that my counter is going to follow would be $0 \rightarrow 1 \rightarrow 3 \rightarrow 2 \rightarrow 6 \rightarrow 7 \rightarrow 5 \rightarrow 4 \rightarrow 12 \rightarrow 13 \rightarrow 15 \rightarrow 14 \rightarrow 10 \rightarrow 11 \rightarrow 9 \rightarrow 8 \rightarrow 0$.

Q_3	Q_2	Q_1	Q_0	Decimal Num
0	0	0	0	0
0	0	0	1	1
0	0	1	1	3
0	0	1	0	2
0	1	1	0	6
0	1	1	1	7
0	1	0	1	5
0	1	0	0	4
1	1	0	0	12
1	1	0	1	13
1	1	1	1	15
1	1	1	0	14
1	0	1	0	10
1	0	1	1	11
1	0	0	1	9
1	0	0	0	8

Since total number of states = $16 = 2^4$, thus total 4 SR flipflops would be required.

1.2 Simplification using K-Maps

Q_3Q_2	Q_1Q_0			
	00	01	11	10
00	1	X	0	0
01	0	0	X	1
11	1	X	0	0
10	0	0	X	1

Figure 1: K-Map for S_0

Q_3Q_2	Q_1Q_0			
	00	01	11	10
00	0	0	1	X
01	X	1	0	0
11	0	0	1	X
10	X	1	0	0

Figure 2: K-Map for R_0

From the k-maps, for first flipflop, the simplified expressions are

$$S_0 = \bar{Q}_3\bar{Q}_2\bar{Q}_1 + \bar{Q}_3Q_2Q_1 + \bar{Q}_1Q_2Q_3 + \bar{Q}_2Q_3Q_1 \implies S_0 = \bar{Q}_3 \oplus \bar{Q}_2 \oplus \bar{Q}_1$$

$$R_0 = \bar{Q}_3\bar{Q}_2Q_1 + \bar{Q}_1\bar{Q}_2Q_3 + \bar{Q}_3\bar{Q}_1Q_2 + Q_3Q_2Q_1 \implies R_0 = Q_3 \oplus Q_2 \oplus Q_1$$

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	1	X	X
	01	0	0	0	X
	11	0	1	X	X
	10	0	0	0	X

Figure 3: K-Map for S_1

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	X	0	0	0
	01	X	X	1	0
	11	X	0	0	0
	10	X	X	1	0

Figure 4: K-Map for R_1

From the k-maps, for second flipflop, the simplified expressions are

$$S_1 = Q_3Q_2Q_0 + \bar{Q}_3\bar{Q}_2Q_0 \implies S_1 = Q_0 \cdot (\bar{Q}_3 \oplus Q_2)$$

$$R_1 = \bar{Q}_3Q_2Q_0 + \bar{Q}_2Q_3Q_0 \implies R_1 = Q_0 \cdot (Q_3 \oplus Q_2)$$

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	0	0	1
	01	X	X	X	X
	11	X	X	X	0
	10	0	0	0	0

Figure 5: K-Map for S_2

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	X	X	X	0
	01	0	0	0	0
	11	0	0	0	1
	10	X	X	X	X

Figure 6: K-Map for R_2

From the k-maps, for third flipflop, the simplified expressions are

$$S_2 = \bar{Q}_0Q_1\bar{Q}_3$$

$$R_2 = \bar{Q}_0Q_1Q_3$$

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	0	0	0	0
	01	1	0	0	0
	11	X	X	X	X
	10	0	X	X	X

Figure 7: K-Map for S_3

		Q_1Q_0			
		00	01	11	10
Q_3Q_2	00	X	X	X	X
	01	0	X	X	X
	11	0	0	0	0
	10	1	0	0	0

Figure 8: K-Map for R_3

From the k-maps, for third flipflop, the simplified expressions are

$$S_3 = Q_2\bar{Q}_0\bar{Q}_1$$

$$R_3 = \bar{Q}_2\bar{Q}_0\bar{Q}_1$$

1.3 Circuit Diagram

The circuit diagram for the counter using the simplified expressions from above, is:

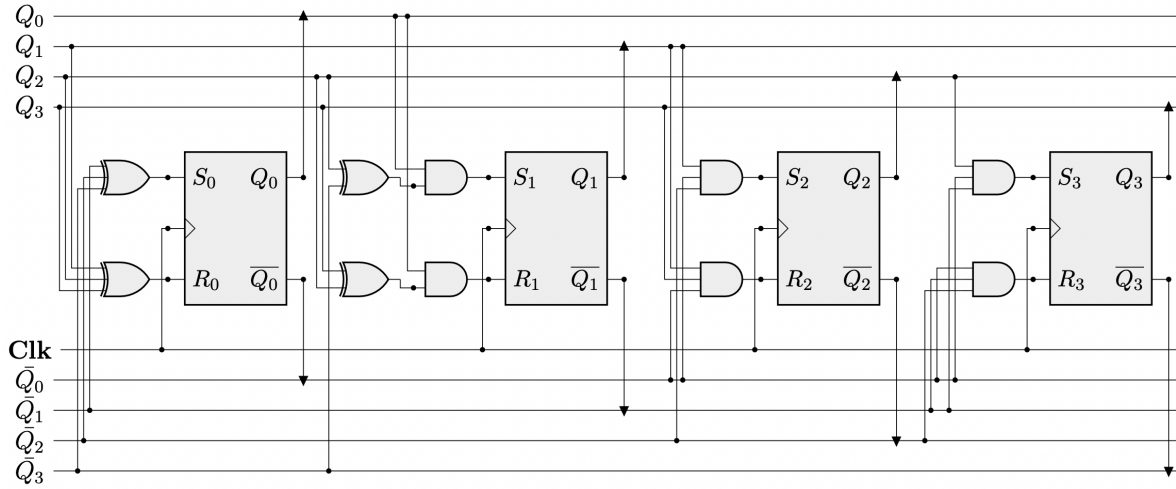


Figure 9: Circuit Diagram

1.4 Verilog Simulation

The code is implemented in such a way that flipflops behave as postive edge triggered not latches.

1.4.1 Code


The code for the implementation of the SR flipflop file (design.v) :

```
1 module SRFlipFlop(S,R,clock,Q,Qbar);
2 input S,R,clock;
3 output reg Q=0,Qbar=1;
4
5 always@(posedge clock)
6 begin
7     if(S & ~R)
8     begin
9         Q <= 1;
10        Qbar <= 0;
11    end
12    else if(~S & R)
13    begin
14        Q <= 0;
15        Qbar <= 1;
16    end
17    else if(~S & ~R)
18    begin
19        Q <= Q;
20        Qbar <= Qbar;
21    end
22    else if(S & R)
23    begin
24        Q <= 1'bx;
25        Qbar <= 1'bx;
26    end
27 end
28 endmodule
```

The code for the testbench file (main.v) :

```
1 `timescale 1s/100ms
2 `include "design.v"
3
4 module main();
5
6 reg clk;
7 wire q0,q0bar,q1,q1bar,q2,q2bar,q3,q3bar;
8
9 //Instantation of flip flops
10 SRFlipFlop ff0(q1bar ^ q2bar ^ q3bar,q1 ^ q2 ^ q3,clk,q0,q0bar);
11 SRFlipFlop ff1(q0 & (q3bar ^ q2),q0 & (q3 ^ q2),clk,q1,q1bar);
12 SRFlipFlop ff2(q3bar & q1 & q0bar,q3 & q1 & q0bar,clk,q2,q2bar);
13 SRFlipFlop ff3(q2 & q1bar & q0bar,q2bar & q1bar & q0bar,clk,q3,q3bar);
14
15 initial
16 begin
17 $monitor("CLK=%b,q3=%b,q2=%b,q1=%b,q0=%b",clk,q3,q2,q1,q0);
18 $dumpfile("design.vcd");
19 $dumpvars(0,main);
20   clk=0; //intitially clock=0;
21   #160; //simulation time (enough for all states to occur)
22   $finish;
23 end
24 always
25   #5 clk = ~clk; //changing clock after every 5s
26 endmodule
```

1.4.2 Waveform plot

 

2 Synchronous Ring Counter

2.1 Introduction

From the table it can be observed that there are total 15 different states of the counter. Also since $2^4 \geq 15$, hence total number of D flip-flops required would be 4.

Since the connections for the ring counter are such that for all intermediate flipflops, output of one flipflop is the input for next flipflop, and for the flipflop it can take any combination of the current states.

Thus from the K-map for D_3 , the simplified expression obtained is :

$$D_3 = Q_1\bar{Q}_0 + Q_0\bar{Q}_1 \implies D_3 = Q_1 \oplus Q_0$$

Q_3Q_2 \ Q_1Q_0	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

2.2 Circuit Diagram

Thus the circuit diagram for this ring counter would be:

Figure 10: K-Map for D_3

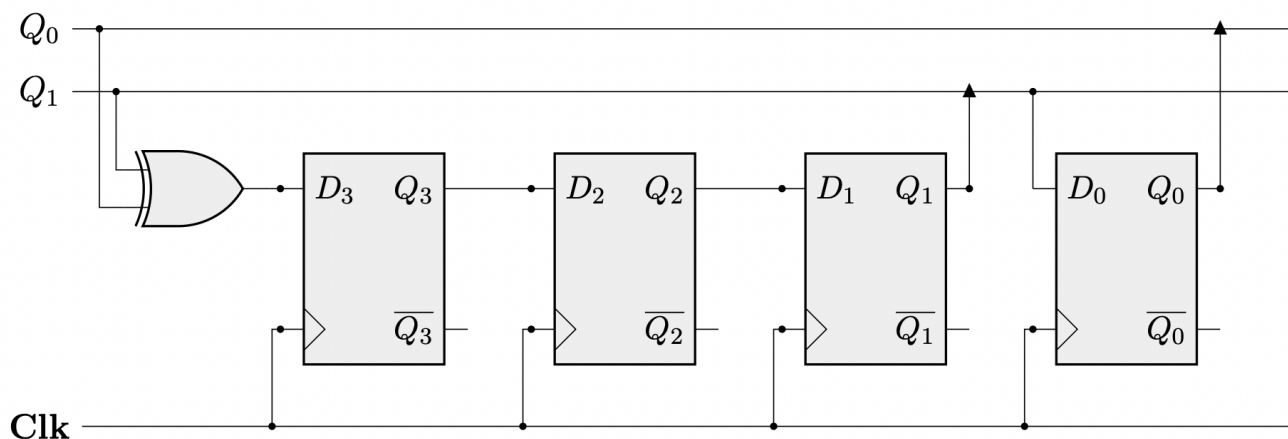


Figure 11: Circuit Diagram

2.3 Verilog Simulation

According to my entry number, the initial state should be:

$$Q_3 = 1, Q_2 = 0, Q_1 = 0, Q_0 = 0$$

The preset parameter is here used to input the initial condition to flipflop. It is configured as low active (hence when preset=0, then $Q = 1$). The D flipflops are coded in such a way that they behave as positive edge triggered not latches.

2.3.1 Code


The code for the implementation of the D flipflop file (design.v):

```
1 module DFlipFlop(D,clock,preset,Q,Qbar);
2 input D,clock,preset;
3 output reg Q,Qbar;
4
5 initial
6 begin
7     if(~preset)
8     begin
9         Q=1;Qbar=0;
10    end
11    else
12    begin
13        Q=0;Qbar=1;
14    end
15 end
16
17 always@(posedge clock)
18 begin
19     Q <= D;
20     Qbar <= ~D;
21 end
22 endmodule
```

The code for the testbench file (main.v):

```
1 `timescale 1s/100ms
2 `include "design.v"
3
4 module main();
5
6 reg clk;
7 wire q0,q1,q2,q3,q3bar,q2bar,q1bar,q0bar;
8
9 //Instantating the flip flops with respective intial values
10 DFlipFlop ff3(q1^q0,clk,1'b0,q3,q3bar);
11 DFlipFlop ff2(q3,clk,1'b1,q2,q2bar);
12 DFlipFlop ff1(q2,clk,1'b1,q1,q1bar);
13 DFlipFlop ff0(q1,clk,1'b1,q0,q0bar);
14
15 initial
16 begin
17     $monitor("CLK=%b,q3=%b,q2=%b,q1=%b,q0=%b",clk,q3,q2,q1,q0);
18     $dumpfile("design.vcd");
19     $dumpvars(0,main);
20     clk=0; //intitially clock=0;
21     #150; //simulation time
22     $finish;
23 end
24 always
25     #5 clk = ~clk; //changing clock after every 5s
26 endmodule
```

2.3.2 Waveform plot

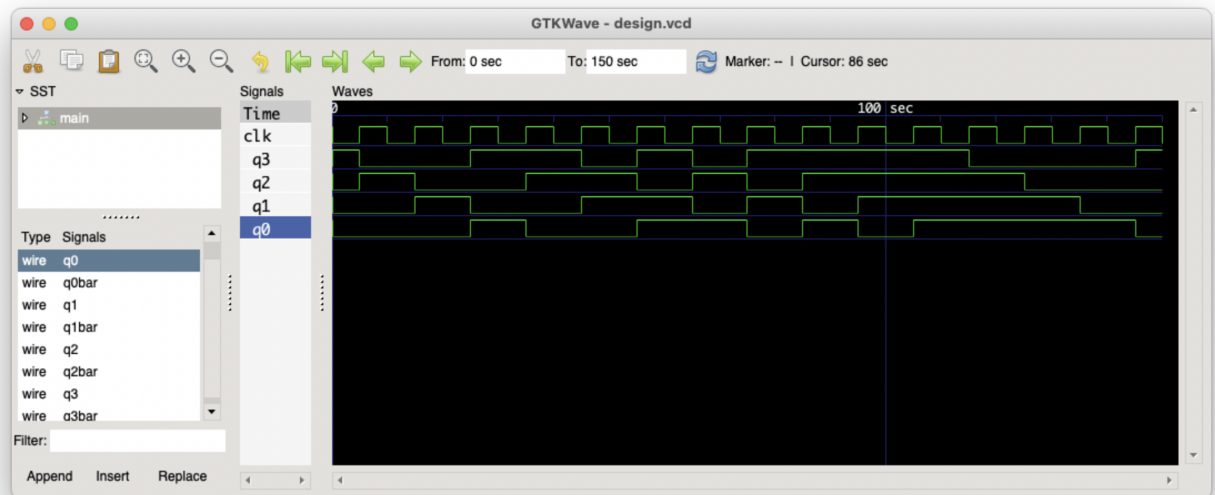

2.4 Further Analysis

Since the cycle of the counter consists of only 15 states, and the state which isn't getting covered in the cycle is 0000. If the counter starts from state 0000, then this state would keep on repeating for every clock impulse and the counter would get stuck in an lockout condition. Whereas if it starts from any other state, then the counter would follow the sequence given in the question, covering each one of the 15 states once before getting back to initial state.

3 Code Files Link

The respective code files to run the simulation for both the Synchronous Gray Code Counter and Synchronous Ring Counter can be downloaded from [here](#).